

CPSC 121: Models of Computation

Unit 1: Propositional Logic

George Tsiknis

Based on slides by Patrice Belleville and Steve Wolfman

Pre-Lecture Learning Goals

- By the start of the class, you should be able to:
 - Translate back and forth between simple natural language statements and propositional logic.
 - Evaluate the truth of propositional logic statements using truth tables.
 - Translate back and forth between propositional logic statements and circuits that assess the truth of those statements.

Unit 1 - Propositional Logic

2

Quiz 1 Feedback

■

- We will discuss the open-ended question a bit later.

Unit 1 - Propositional Logic

3

In-Class Learning Goals

- By the end of this unit, you should be able to:
 - Build computational systems to solve real problems, using both propositional logic expressions and equivalent digital logic circuits.
 - The light switches problem from the 1st online quiz.
 - The 7- or 4-segment LED displays we will discuss in class.
- Building ground work for the Course Big Goals:
 - How do we model computational systems?
 - How do we build devices to compute?

Unit 1 - Propositional Logic

4

Making a Truth Table

- Note: when you write a truth table, always list the combinations in the same order.
 - For instance, with 3 variables
 - the first column contains 4 **false** followed by 4 **true**.
 - the second column contains 2 **false**, 2 **true**, 2 **false**, 2 **true**.
 - and the third column alternates **false** with **true**.
 - With k variables, the first column has 2^{k-1} **false** and then 2^{k-1} **true**, the second column has 2^{k-2} **false** and then 2^{k-2} **true** (twice), etc.
- Another way is to
 - start with the last column and one variable which will be assigned **F** and **T**
 - add one variable at a time duplicating what you have so far and setting the new variable to **F** for the first copy and **T** for the second


Circuits to Logic Expressions

- How do we find the logical expression that corresponds to a circuit's output?
 - First we write the operator for the gate that produces the circuit's output.
 - The operator's left argument is the expression that corresponds to the circuit for the first input of that gate.
 - The operator's right argument is the expression that corresponds to the circuit for the second input of that gate.
 - Build the logical expression for the left and right argument the same way.

This is our First algorithm!

Example 1


- What does this circuit compute?

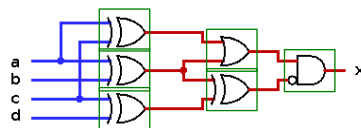

$$((a \oplus c) \vee (a \oplus b)) \wedge \neg((a \oplus b) \oplus c \oplus d)$$

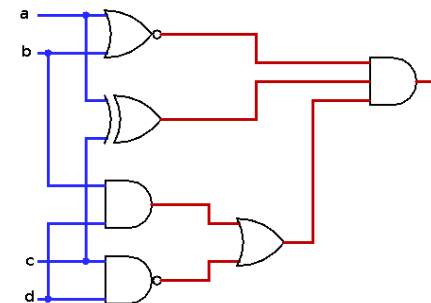
Example 2

- What logical expression corresponds to the following circuit?



Problem: Three-Switch

- Design a circuit that changes the state of the light whenever any of the switches that control it is flipped.
- Ideally your solution would work with any number!

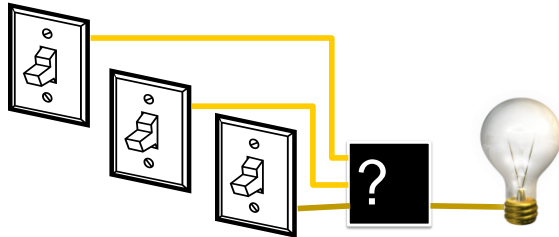

Unit 1 - Propositional Logic

9

How do we approach this?



- **Try to understand the “story”:**
 - what are the inputs and outputs?
- **Formalize the problem:**
 - “Let a,b,c represent 3 switches from left to right”
- **Solve in propositional logic:**
 - may create a truth table with the inputs and outputs
- **Try a simpler problem:**
 - start with 1 switch; then try 2; then try 3 switches.
 - see if we can generalize to n switches.
- **Test your answer:**
 - try some cases, or check some properties

Unit 1 - Propositional Logic

10

One Switch



- Identifying inputs/outputs: consider these:
 - **Input₁**: the switch flipped
 - **Input₂**: the switch is on
 - **Output₁**: the light is on
 - **Output₂**: the light changed state
- Which are most useful for this problem?
 - Input₁** and **Output₁**
 - Input₁** and **Output₂**
 - Input₂** and **Output₁**
 - Input₂** and **Output₂**
 - None of these

Unit 1 - Propositional Logic

11

One Switch



- Let's use:
 - S = switch is on
 - out = light is on
- Truth table:
- Which of the following circuits solves the problem?
 - 1.
 - 2.
 - 3.

Unit 1 - Propositional Logic

12

Two Switches



- Make sure we understand the problem first.
- Is the light on or off when both switches are “on”?
 - A. On in every correct solution.
 - B. Off in every correct solution.
 - C. Depends, but a correct solution should always do the same thing with the same settings for the switches..
 - D. Depends, and a correct solution might do different things at different times with the same settings for the switches.
 - E. Neither on nor off.

Two Switches




- Circuit design tip: if you are not sure where to start while designing a circuit,
 - First build the truth table.
 - Then turn it into a circuit.
- For the two switches problem:
 - We can decide arbitrarily what the output is when all switches are OFF.
 - This determines the output for all other cases!
 - Let's see how...
- Truth table (suppose light OFF when all switches are OFF):

Two Switches



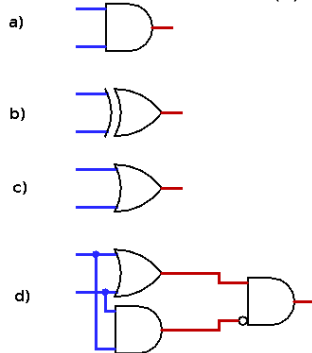- Two switches: which circuit(s) work(s) ?



Three Switches



- Fill in the circuit's truth table:
- Which output column(s) is(are) correct ?

s_1	s_2	s_3	A out	B out	C out	D out	E None of them
T	T	T	T	F	F	T	
T	T	F	F	T	T	F	
T	F	T	F	T	F	T	
T	F	F	T	F	T	F	
F	T	T	F	T	F	T	
F	T	F	T	F	T	F	
F	F	T	T	F	F	T	
F	F	F	F	T	T	F	

Three Switches




- Suppose we decided to have the light OFF when all switches are OFF. What pattern do we observe?
 - The light is ON if
- What is the formula for it?
 -
- Now to generalize to n switches...
 - What do you think the answer is?
 -
- How can we convince ourselves that it is correct?
 - Mathematical induction

7-Segment LED Display



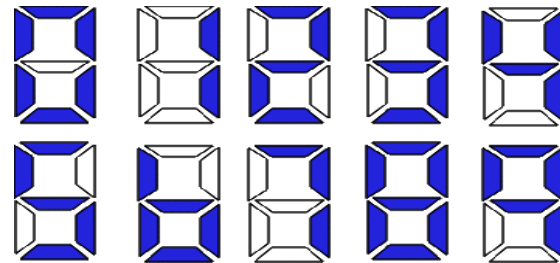- **Problem:** design a circuit that displays the numbers 0 through 9 using seven LEDs (lights) in the shape illustrated below.



7-Segment LED Display



- Understanding the story:
How many inputs *to our circuit* are there?
- a. One
- b. Seven
- c. Ten
- d. Four
- e. None of these

7-LED Display



- **Problem:** Design a circuit that displays the numbers 0 through 9 using seven LEDs (lights) in the shape illustrated above.
- **First: what's the circuit's job?**
 -

7-LED Display–Input **Values**



- How many different values (messages) must the circuit understand?

(This is **different than** “how many inputs are there”.)

- a. One
- b. Seven
- c. Ten
- d. Four
- e. None of these

21

7-LED Display-Input **Lines**



- How many different “parameters” (wires) carry those messages?

(Not *quite* parameter like in CPSC 110... more like an input wire).

- a. One
- b. Seven
- c. Ten
- d. Four
- e. None of these

22

7-LED Display-Inputs



- How do we represent the inputs?

- Use ? logical (true/false) values.
- Each integer represented by 1 specific combination.
- Could we do this randomly?
 - Yes!
- But we won't
 - How many of you know about binary representation?

- How many values we can represent with

- 1 propositional variable :
- 2 propositional variables :
- 3 " " :
- n " " :

Unit 1 - Propositional Logic

23

7-LED Display-Representing Inputs



- Here's how we will represent the inputs:

#	a	b	c	d
0	F	F	F	F
1	F	F	F	T
2	F	F	T	F
3	F	F	T	T
4	F	T	F	F
5	F	T	F	T
6	F	T	T	F
7	F	T	T	T
8	T	F	F	F
9	T	F	F	T
...				

Notice the order: F's first.

Unit 1 - Propositional Logic

24

7-LED Display-Outputs




■ Understanding Outputs:

■ How many outputs are there?

- 1
- 4
- 7
- 10
- None of the above

Simulate 7-LED Display

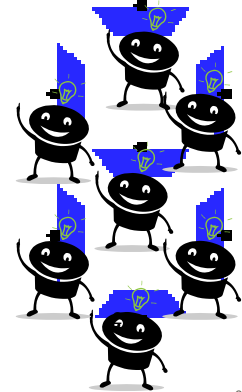- Let's simulate it with people (raising their hands) ...
- Which other person's algorithm do you need to know about?
 - No one else's
 - Your neighbours
 - The person opposite to you
 - Everybody else's
 - None of the above.




Analyzing One Segment

■ What's the truth table for the lower-left segment?

#	a	b	c	d	a. out	b. out	c. out	d. out	e. out
0	F	F	F	F	F	F	F	F	T
1	F	F	F	T	T	T	F	F	T
2	F	F	T	F	F	F	T	T	F
3	F	F	T	T	T	T	F	F	T
4	F	T	F	F	F	T	F	F	T
5	F	T	F	T	T	T	F	F	T
6	F	T	T	F	F	F	T	T	F
7	F	T	T	T	T	T	F	F	T
8	T	F	F	F	F	F	T	T	F
9	T	F	F	T	T	T	F	F	T

None of these.

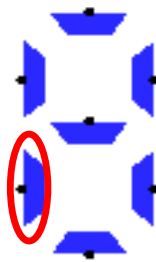

Analyzing One Segment



- From the truth table, we can make an expression for each **true** row and **OR** them together.

#	a	b	c	d	out
0	F	F	F	F	T
1	F	F	F	T	F
2	F	F	T	F	T
3	F	F	T	T	F
4	F	T	F	F	F
5	F	T	F	T	F
6	F	T	T	F	T
7	F	T	T	T	F
8	T	F	F	F	T
9	T	F	F	T	F

Which logical statement is true only in this row?

- $\sim a \vee \sim b \vee c \vee \sim d$
- $a \wedge b \vee c \wedge d$
- $\sim a \wedge \sim b \wedge c \wedge \sim d$
- $a \wedge b \wedge \sim c \wedge d$
- None of these

Analyzing One Segment

- Let's complete the expression for the lower-left segment

#	a	b	c	d	out
0	F	F	F	F	T
1	F	F	F	T	F
2	F	F	T	F	T
3	F	F	T	T	F
4	F	T	F	F	F
5	F	T	F	T	F
6	F	T	T	F	T
7	F	T	T	T	F
8	T	F	F	F	T
9	T	F	F	T	F

$($ $) \vee$
 $($ $) \vee$
 $($ $) \vee$
 $)$

29

Alternative to Table with Many Ts

- We can use the F rows and negate the statement!

#	a	b	c	d	out
0	F	F	F	F	T
1	F	F	F	T	T
2	F	F	T	F	T
3	F	F	T	T	T
4	F	T	F	F	T
5	F	T	F	T	F
6	F	T	T	F	F
7	F	T	T	T	T
8	T	F	F	F	T
9	T	F	F	T	T

Which of these correctly models this LED?

- $\sim(\sim a \wedge b \wedge \sim c \wedge d) \vee \sim(\sim a \wedge b \wedge c \wedge \sim d)$
- $\sim(a \wedge \sim b \wedge c \wedge \sim d) \vee \sim(a \wedge \sim b \wedge \sim c \wedge d)$
- $\sim[(\sim a \wedge b \wedge \sim c \wedge d) \vee (\sim a \wedge b \wedge c \wedge \sim d)]$
- $\sim[(a \wedge \sim b \wedge c \wedge \sim d) \vee (a \wedge \sim b \wedge \sim c \wedge d)]$
- None of these

30

Another Way

#	a	b	c	d	out
0	F	F	F	F	T
1	F	F	F	T	F
2	F	F	T	F	T
3	F	F	T	T	F
4	F	T	F	F	F
5	F	T	F	T	F
6	F	T	T	F	T
7	F	T	T	T	F
8	T	F	F	F	T
9	T	F	F	T	F

- Looking back at the bottom-left segment:

- There may be a simpler proposition, which will translate into a smaller circuit.
- Can you find a pattern in the rows for which the segment should be "on"?

Unit 1 - Propositional Logic

31

What is coming up?

- Second online quiz is due on **WEDNESDAY, SEPT 10, 7:00pm.**
- Assigned reading for the quiz:
 - Epp, 4th edition: 2.2
 - Epp, 3rd edition: 1.2
 - Rosen, 6th edition: 1.1 from page 6 onwards.

Unit 1 - Propositional Logic

32

Exercises:

- Prove that our two solutions for the lower-left segment are not logically equivalent.
 - You should do this by providing values for the variables, so the two propositions have different truth values.
 - Why are they both correct solutions, despite that?
- Finish the problem by building circuits for the other 5 segments.
- Design a circuit that takes three bits as input, and outputs the binary representation for their sum.